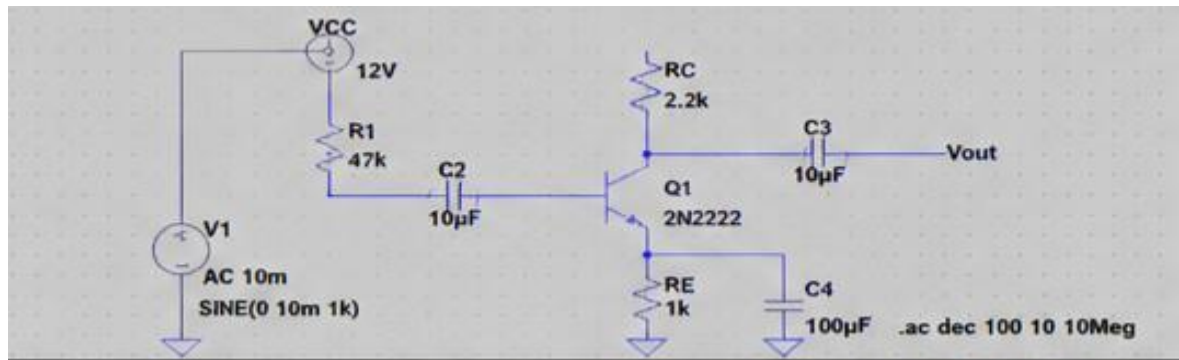



EXPERIMENT – 5

DESIGN AND SIMULATION OF COMMON BASE AMPLIFIER USING LTSPICE SIMULATOR

Circuit Diagram:



Output:

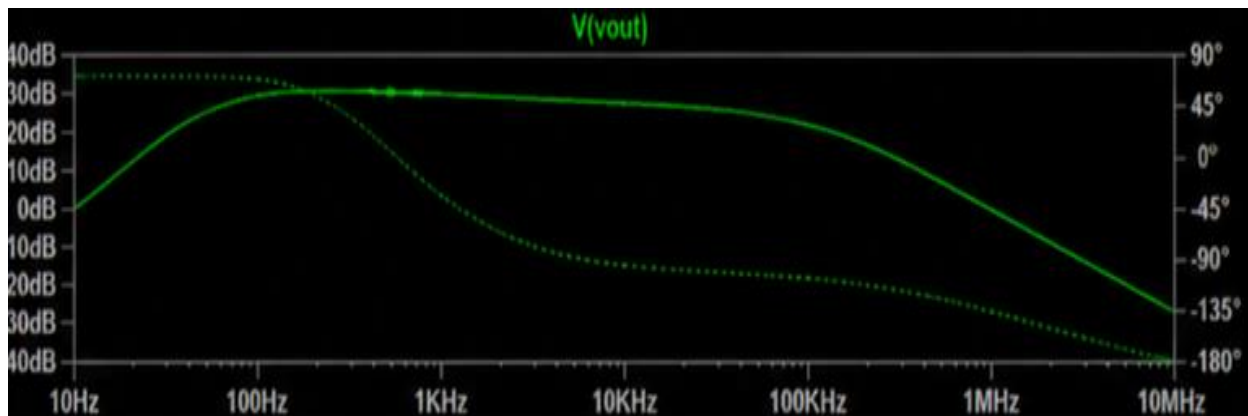


Result:

The frequency response characteristics of the Common Base amplifier were analyzed successfully using LTSpice.


EXPERIMENT – 6

DESIGN AND ANALYSIS OF ASTABLE MULTIVIBRATOR USING BJT

Circuit Diagram:

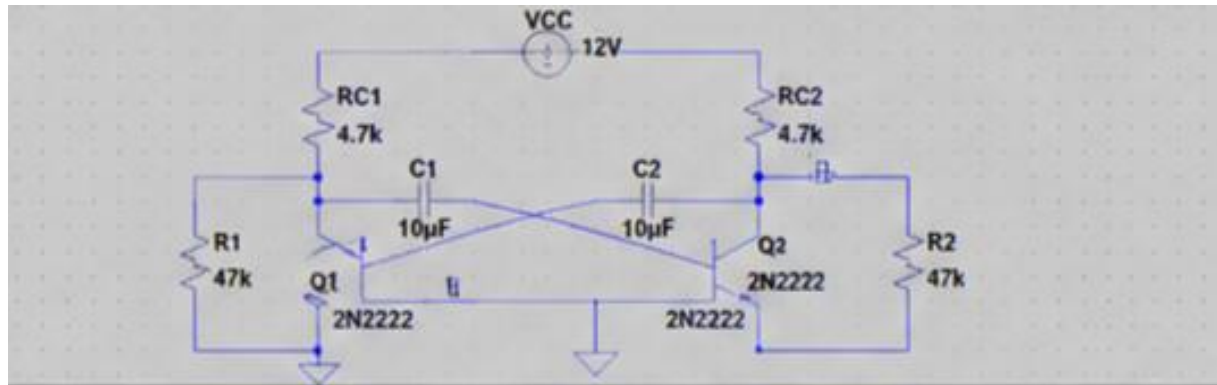

Output:

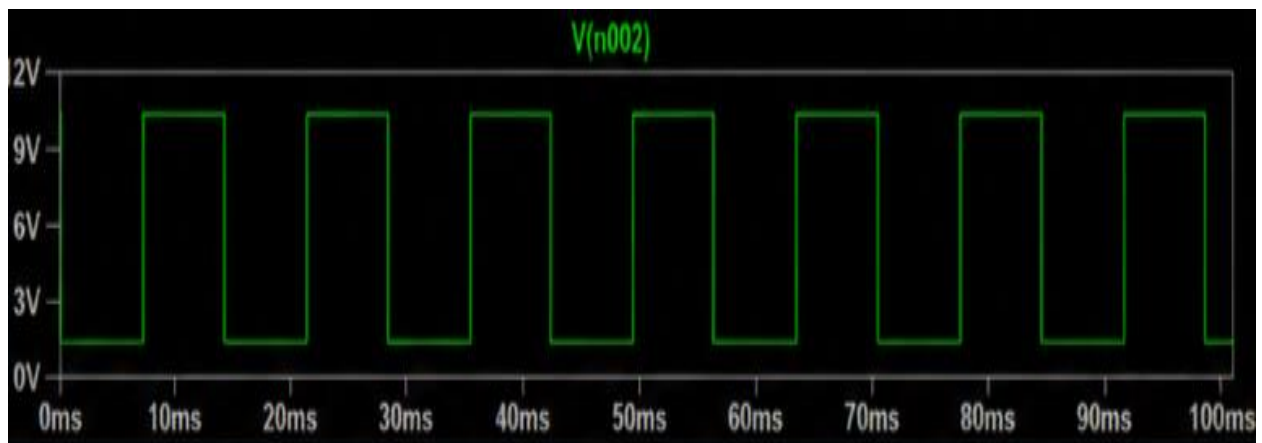


Result:

The duty cycle of the astable multivibrator was determined successfully and verified with theoretical calculations.


EXPERIMENT – 7

DESIGN AND ANALYSIS OF SCHMITT TRIGGER USING LTSPICE

Circuit Diagram :

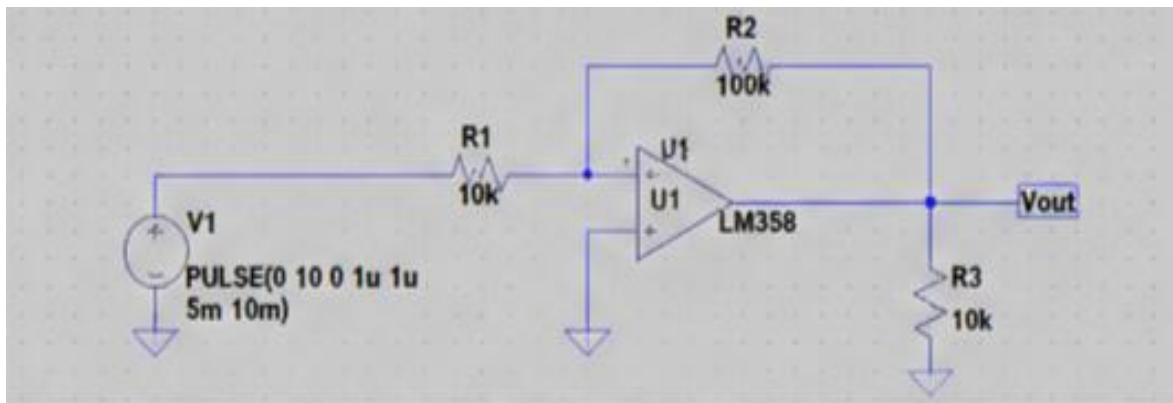

Output:

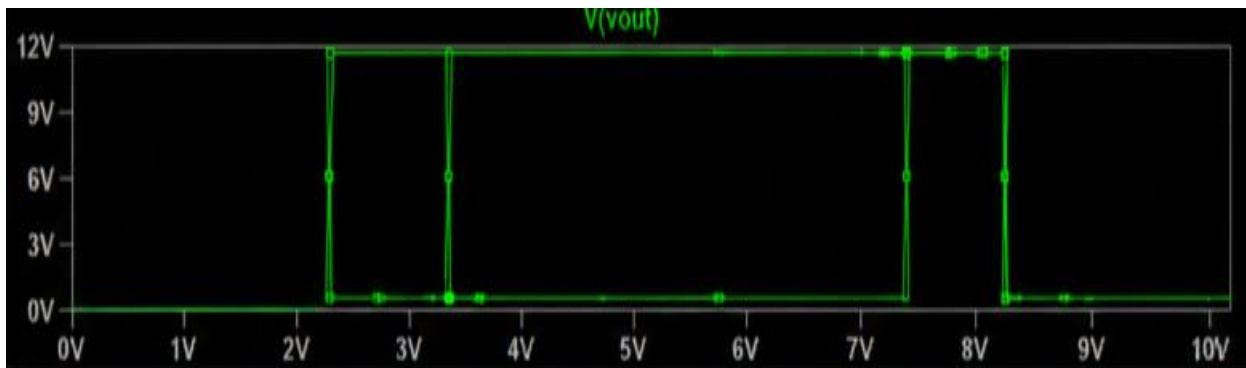


Result:

Thus the plot hysteresis characteristics of a Schmitt Trigger was done.


EXPERIMENT – 8

DESIGN AND SIMULATION OF UJT RELAXATION OSCILLATOR USING LTSPICE

Circuit Diagram :

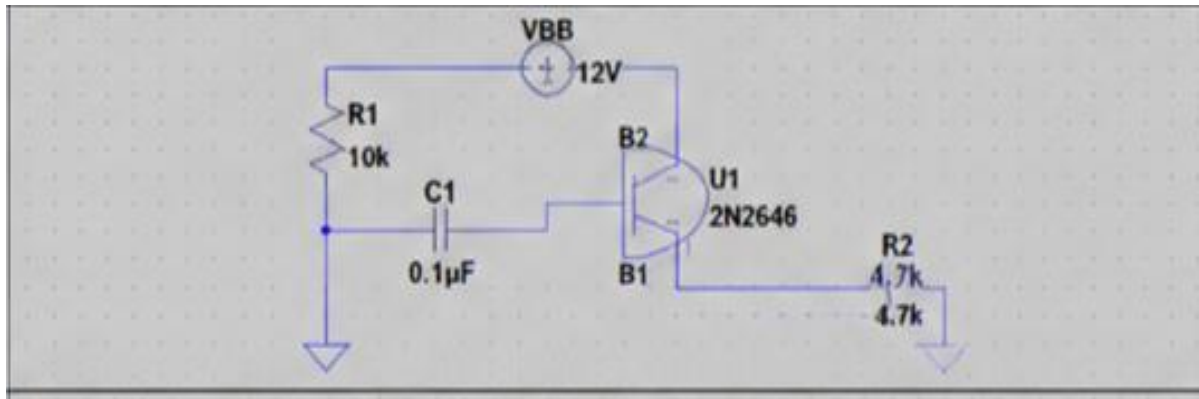

Output:

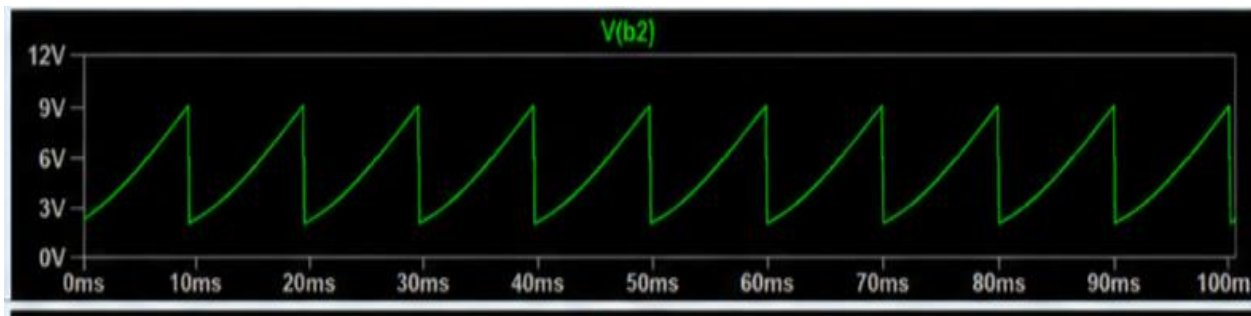


Result:

UJT Relaxation Oscillator using LTSpice was completed and output obtained.


EXPERIMENT – 9

Design of Hartley Oscillator Using PCB Software

Circuit Diagram:

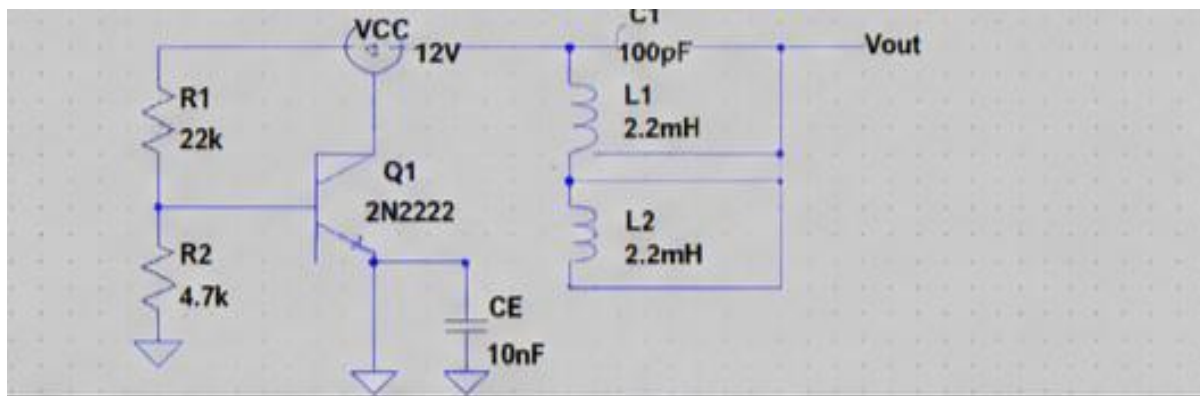

Output:

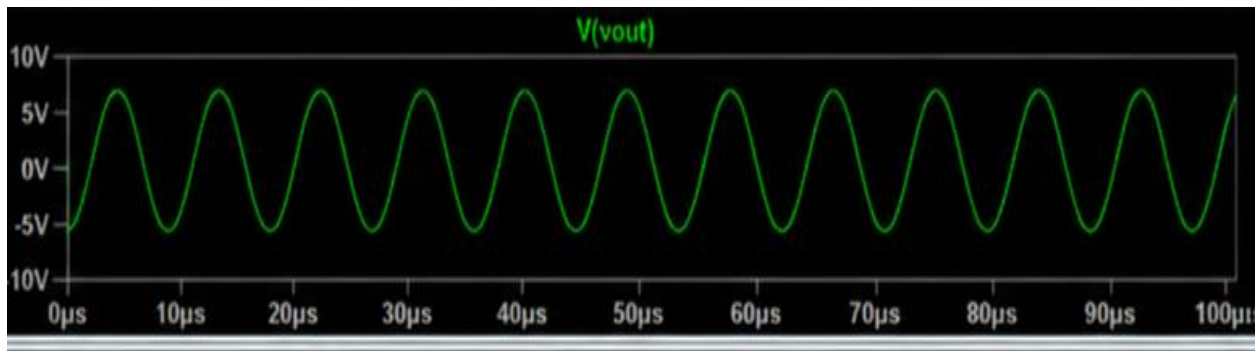


Result:

The Hartley oscillator circuit was successfully designed using PCB software. The PCB layout was Completed and Gerber files were generated for fabrication.


EXPERIMENT – 10

Design of Monostable Multivibrator Using PCB Software

Circuit Diagram:

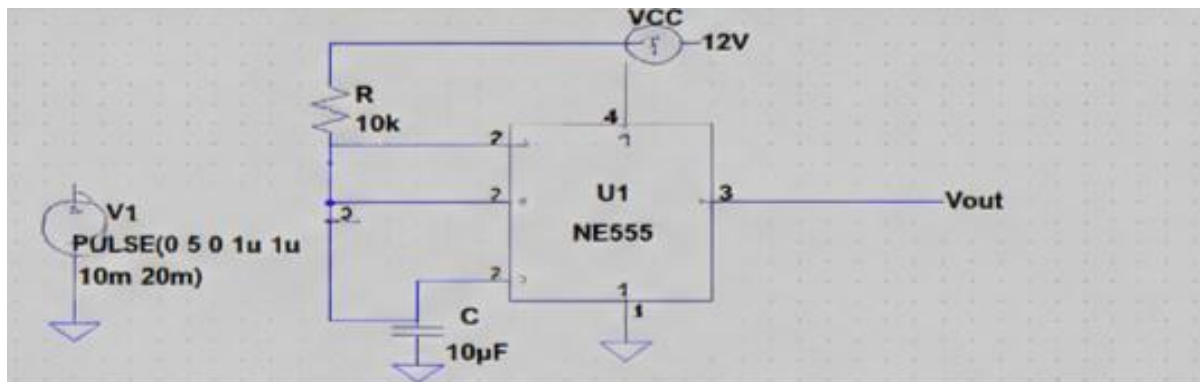

Output:

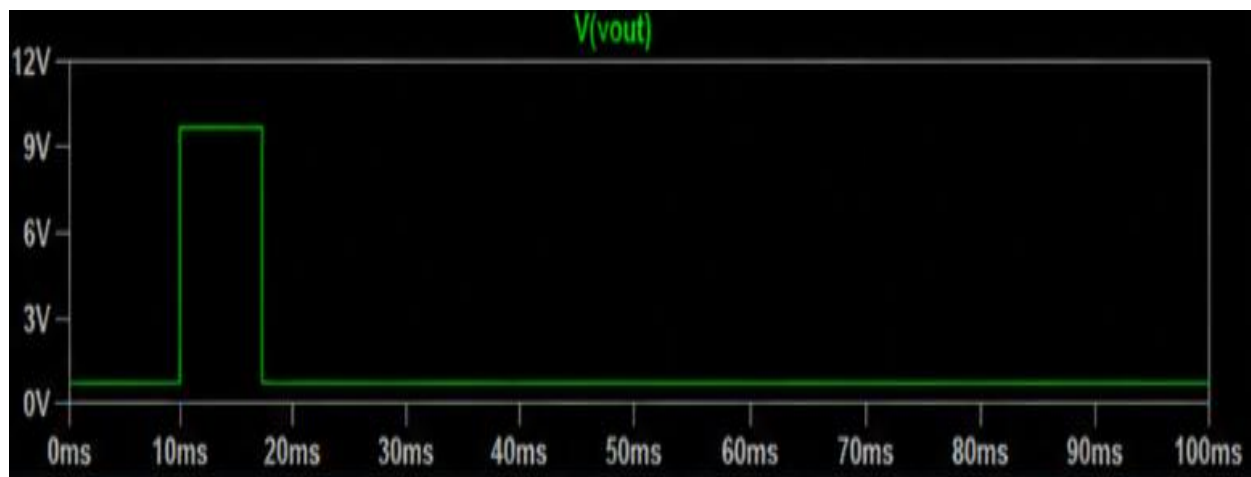

Result:

The Hartley oscillator circuit was successfully designed using PCB software. The PCB layout was completed and Gerber files were generated for fabrication.

